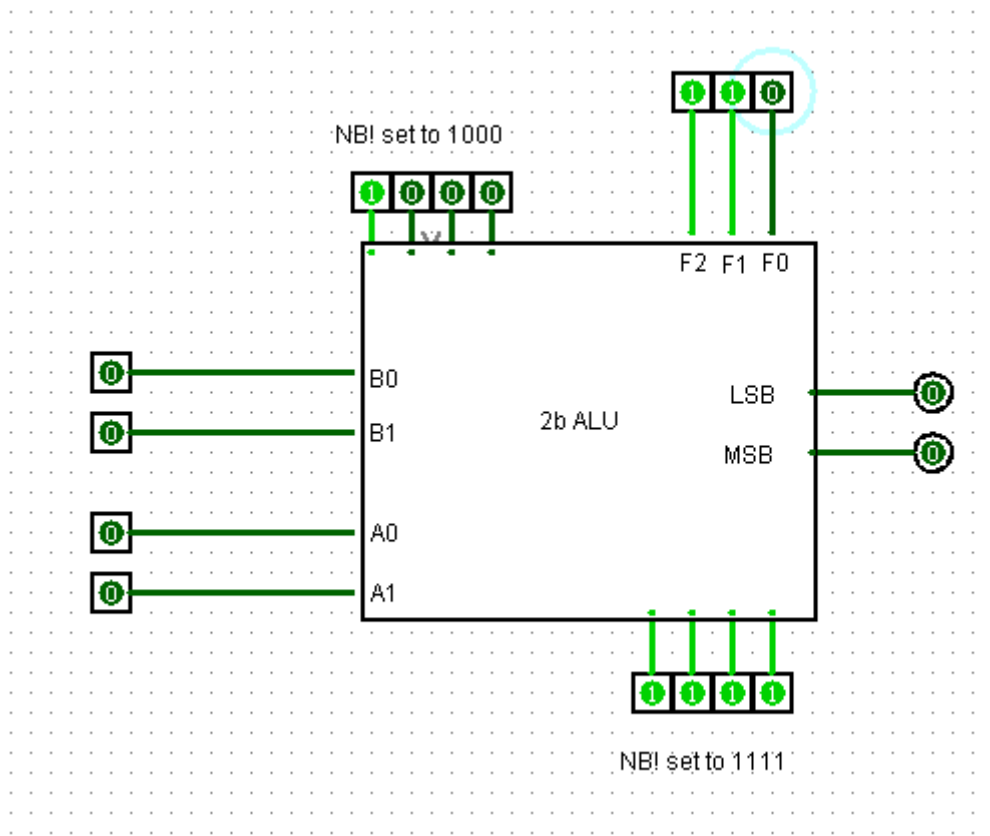



PRAC_5_LPHTUM003_JHRSHA002



ADDER SUBTRACTOR COMPONENT

Addition and subtraction operations are combined into a single circuit. The use of two 1-bit XOR gates allow for the circuit to change from simply computing $A + B$ to $A + \bar{B} + 1$. These operations are activated by the opcodes: $F_2 \rightarrow 0: F_1 \rightarrow 0: F_0 \rightarrow 0$ and $F_2 \rightarrow 0: F_1 \rightarrow 0: F_0 \rightarrow 1$ respectively.

ADDITION

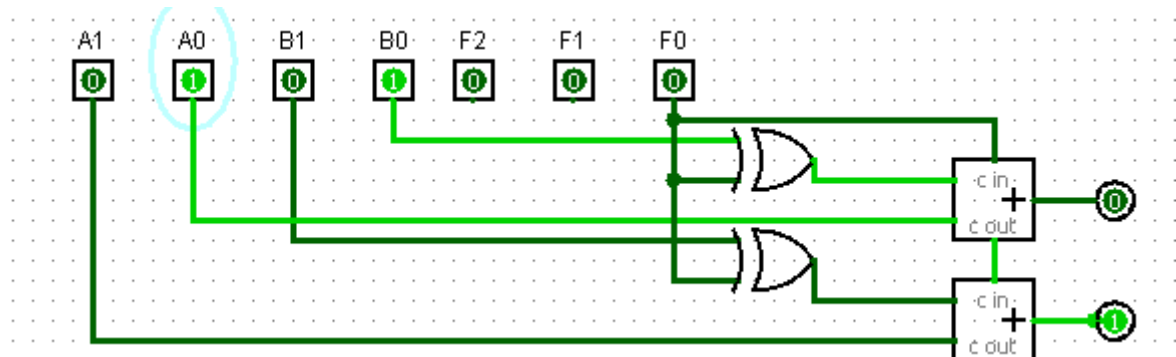


Addition was calculated using two 1-bit full adders the truth table below represents how a single adder operates.

X_1	X_0	C_{in}	C_{out}	S
-------	-------	----------	-----------	-----

0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

SUBTRACTION

 


Subtraction was calculated using two 1-bit full adders and the use of XOR gates to add a constant 1 from the opcode as well as the complement of B. The truth table below represents how a single adder operates when it is used as a subtractor.

X_1	X_0	B_{IN}	D	B_{OUT}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

INCREMENT AND DECREMENT

Increment and decrement operations are combined into a single circuit. The use of two XOR gates allow for the circuit to change from simply computing $A + 1$ to $A + \bar{1} + 1$. These operations are activated by the opcodes: $F_2 \rightarrow 0: F_1 \rightarrow 1: F_1 \rightarrow 0$ and $F_2 \rightarrow 0: F_1 \rightarrow 1: F_0 \rightarrow 1$ respectively.


INCREMENT

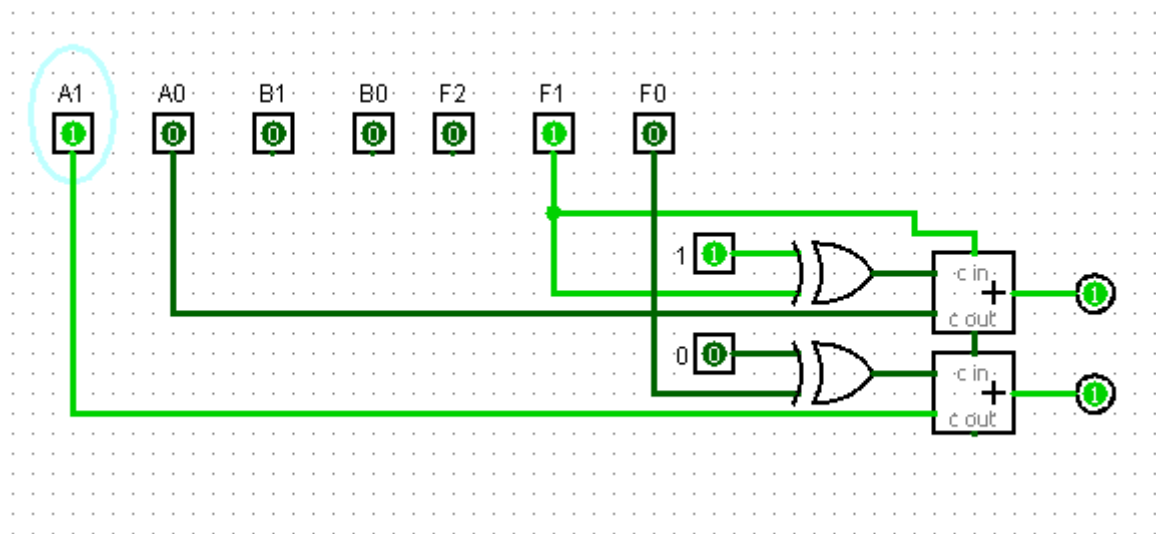

Increment is achieved by using 2 1-bit full adders and having a constant 1 added to each A bit the truth table below represents how a single adder operates in these conditions.

A ₁	A ₀	1	C _{OUT}	S
0	0	1	0	1
0	1	1	1	0
1	1	1	0	0
1	0	1	1	1

DECREMENT

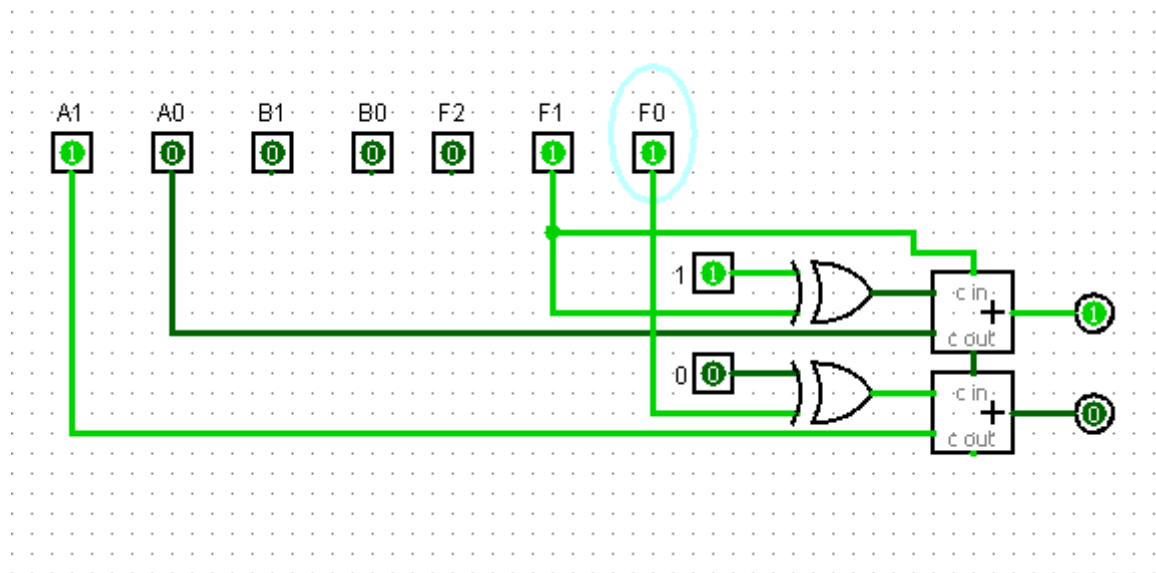

Decrement is achieved by using 2 1-bit full adders and the use of XOR gates to add a constant 1 from the opcode as well as the complement of 1. The truth table below represents how a single adder operates when it is used as a decrementor.


A ₁	A ₀	1	D	B _{OUT}
0	0	1	1	1
0	1	1	0	0
1	1	1	0	0

1	0	1	1	0
---	---	---	---	---

MULTIPLY AND DIVIDE

Multiplication and division operations are combined into a single circuit. A 2-bit logical shifter can be constructed using two 1-bit multiplexers. Six 1-bit multiplexers were used to choose between $A \ll 1$ and $A \gg 1$. These operations are activated by the opcodes: $F_2 \rightarrow 1: F_1 \rightarrow 0: F_1 \rightarrow 0$ and $F_2 \rightarrow 1: F_1 \rightarrow 0: F_1 \rightarrow 1$ respectively.


MULTIPLICATION

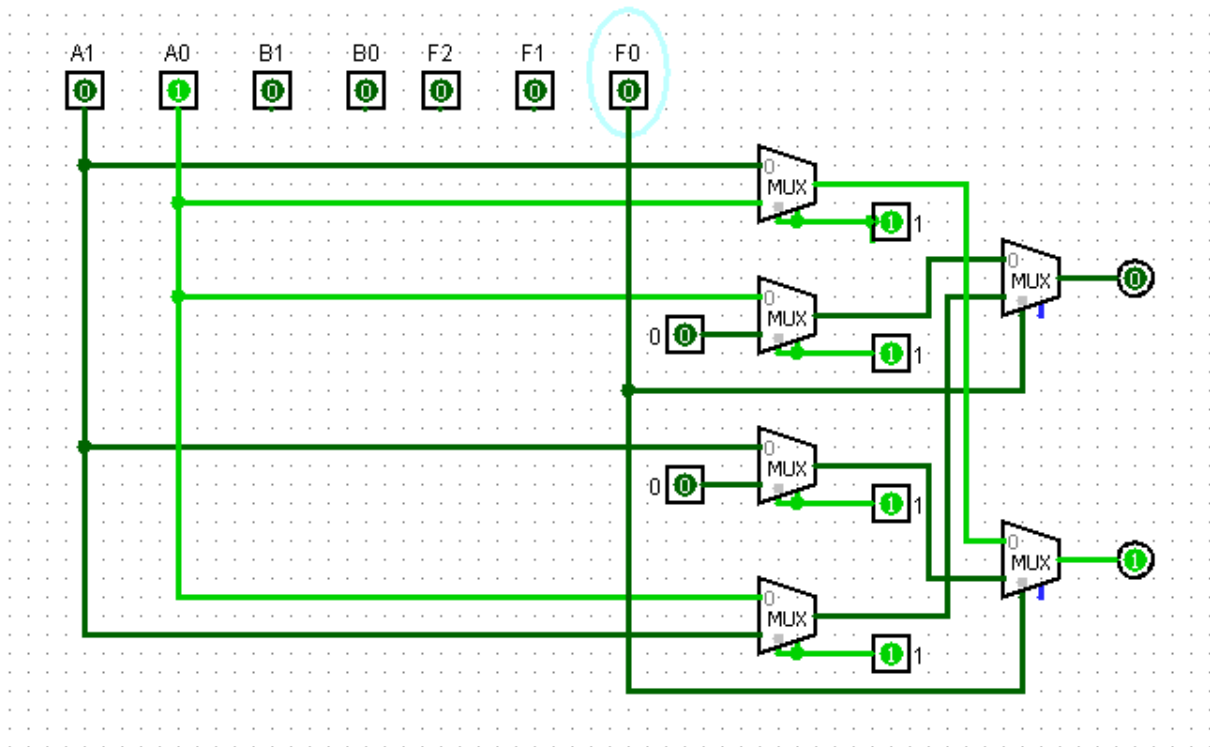

Multiplying by 2 required the combination of six 1-bit multiplexers whereby the last pair of multiplexers have a select of 0. The truth table below represents the results of multiplying by 2

A ₁	A ₀	Y ₁	Y ₀
0	0	0	0
0	1	1	0
1	0	0	0
1	1	1	0

DIVISION

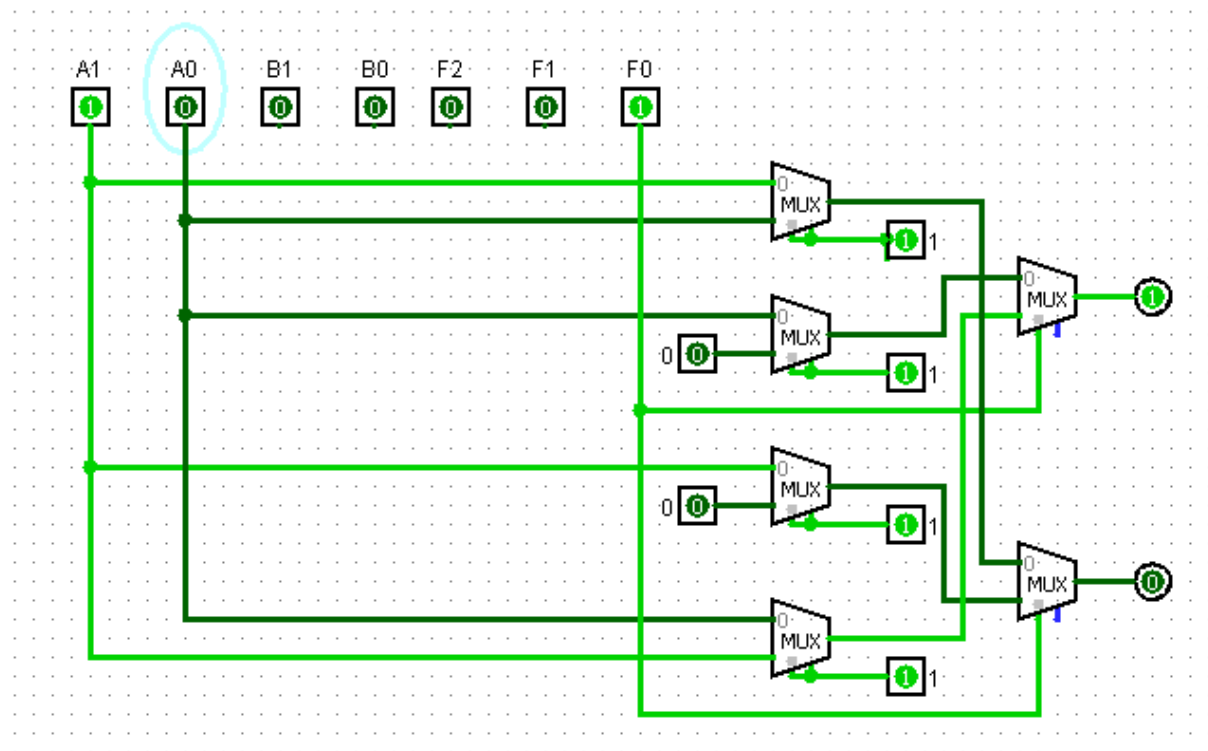


Dividing by 2 required the combination of 6 1-bit multiplexers whereby the last pair of multiplexers have a select of 1. The truth table below represents the results of dividing by 2

A ₁	A ₀	Y ₁	Y ₀
0	0	0	0
0	1	1	0
1	0	0	0
1	1	1	0

BITWISE OPERANDS

Bitwise AND and OR operations are combined into a single circuit. For each bit from A and B we apply both AND and OR operations and have a select line choose which operation to apply to them using a 1-bit multiplexer. These operations are activated by the opcodes: $F_2 \rightarrow 1: F_1 \rightarrow 1: F_1 \rightarrow 0$ and $F_2 \rightarrow 1: F_1 \rightarrow 1: F_1 \rightarrow 1$ respectively.


BITWISE AND

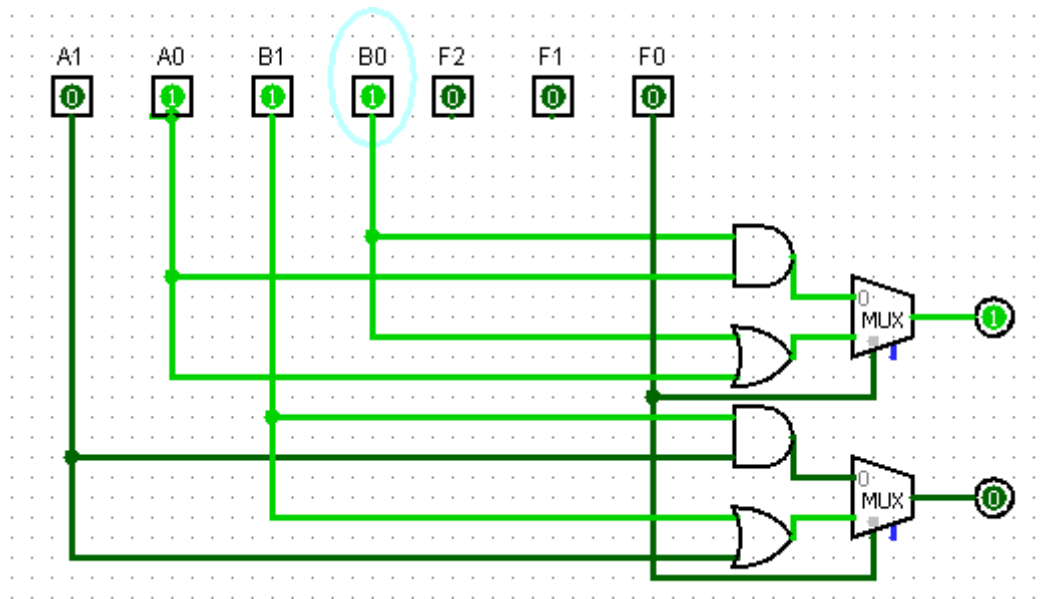

Logical AND is applied to each bit and select is 0. The truth table below represents bitwise A AND B

X_1	X_0	Y
0	0	0
0	1	0
1	0	0
1	1	1

BITWISE OR

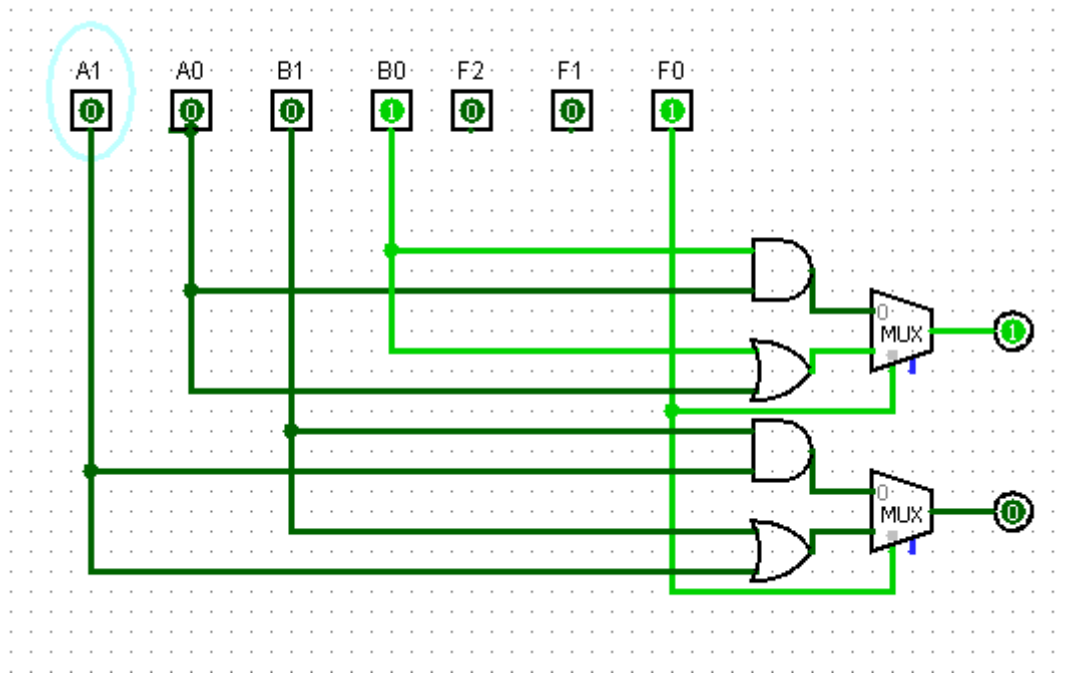

Logical OR is applied to each bit and select is 1. The truth table below represents bitwise A OR B

X_1	X_0	Y
0	0	0
0	1	1
1	0	1
1	1	1